

ECGR 4146 PROJECT 1 PRESENTATION

GROUP 1

MARCH 28, 2018



Dhivya Sivalingam

Ryan Swaim

Andrew Szoke

Swathi Thirunarayanan

PROJECT OVERVIEW

Purpose: to “design, simulate, and synthesize a behavioral embedded microcontroller” in VHDL

Modules created:

Registers

PC

Memory

Decode Logic

IR

IM

ALU

Muxes


Stage Counter

STAGE COUNTER


- Keeps track of which of the three instruction stages the processor is in
- **Stage 0:** Instruction is fetched by IR from the memory through the **datain** bus, PC is incremented
- **Stage 1:** Immediate value is loaded in the Immediate register with value from its memory based on **IRbit7**.
- **Stage 2:** Decode logic decodes the opcodes and corresponding operation is executed.

```
architecture Behavioral of phase_counter is
    signal cnt,tmp : std_logic_vector(1 downto 0);
    signal resetsig : std_logic;
begin
    process(clk,rst)
    begin
        if(rst = '1')then
            cnt <= "11";
        else if(rising_edge(clk)) then
            if(cnt<"10") then
                cnt <= cnt + 1;
            else cnt <= "00";
            -- if(resetsig = '1') then
            --     cnt <= "00";
            end if;
        end if;
    end process;
    -- resetsig <= cnt(1) and cnt(0);
    tmp <= "00" when cnt = "11" else cnt;
    stage <= tmp;
end Behavioral;
```

STAGE COUNTER (cont'd)

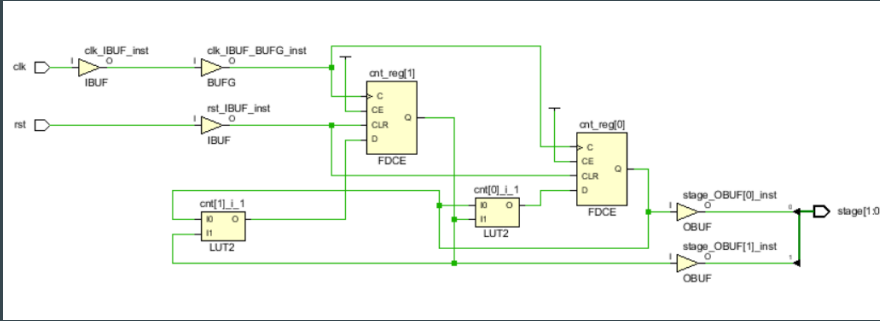


SYNTHESIZED DESIGN

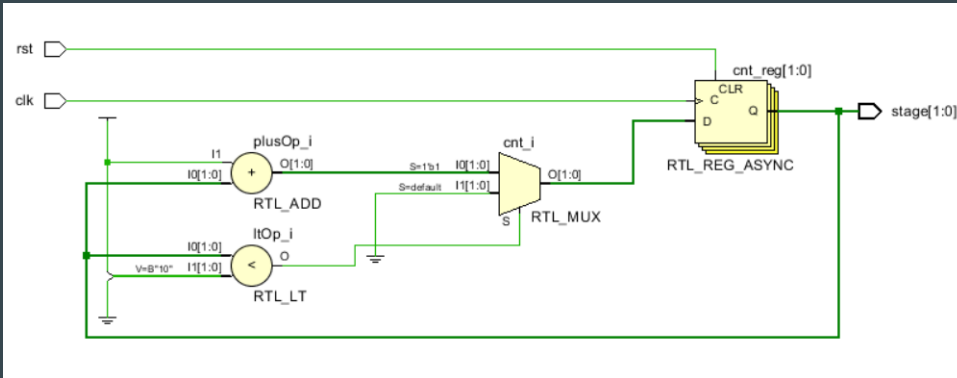

ELABORATED DESIGN

STAGE COUNTER (cont'd)

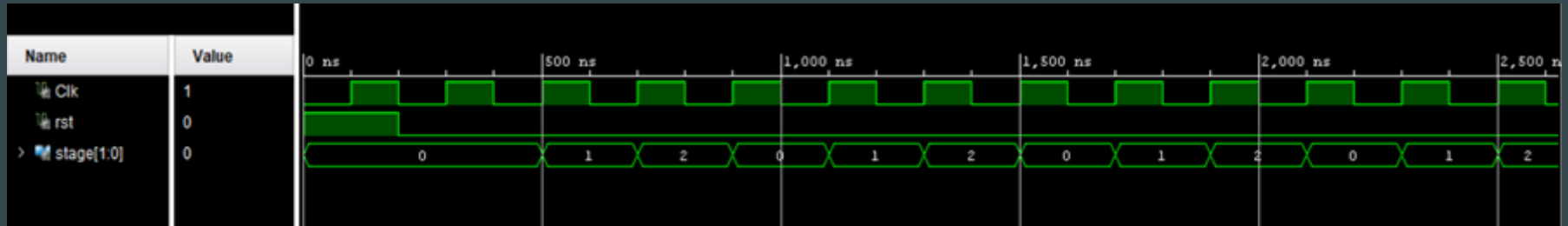


TESTBENCH
RESULTS

MEMORY

- “Array of arrays” of bus width (8 bits)
- Edge-triggered clock and reset inputs
- Toggled by **readwrite** flag from the CPU
- Synchronous write and asynchronous read

```
process(clk,rst) is
begin
  if Rst = '1' then
    -- Clear Memory on Reset
    ramArray <= (others => (others => '0'));
  else
    ramArray(0) <= x"e4";
    ramArray(1) <= x"00";
    ramArray(2) <= x"e0";
    ramArray(3) <= x"80";
    ramArray(4) <= x"48";
    ramArray(5) <= x"88";
    ramArray(6) <= x"0d";
    ramArray(7) <= x"26";
    ramArray(8) <= x"ec";
    ramArray(9) <= x"01";
    ramArray(10) <= x"23";
    ramArray(11) <= x"ff";
    ramArray(12) <= x"04";
    ramArray(13) <= x"d4";
    ramArray(14) <= x"40";
    ramArray(15) <= x"ff";
    ramArray(16) <= x"0f";
    ramArray(128) <= x"02";
    ramArray(129) <= x"01";
    ramArray(130) <= x"00";
    if rising_edge(Clk) then
      if readwrite = '1' then
        ramArray(to_integer(unsigned(Address))) <= Dataout;
      end if;
    end if;
  end if;
end process;
Datain <= ramArray(to_integer(unsigned(Address)));
end RAM;
```

MEMORY (cont'd)

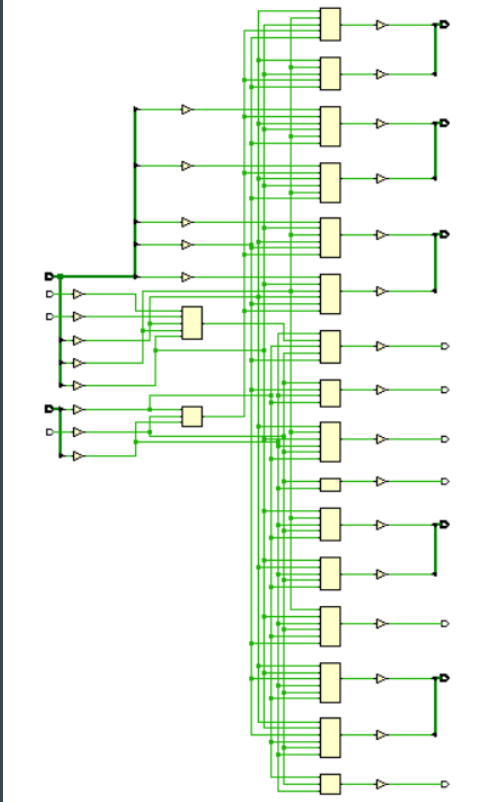


SYNTHESIZED
DESIGN



ELABORATED
DESIGN


MEMORY (cont'd)

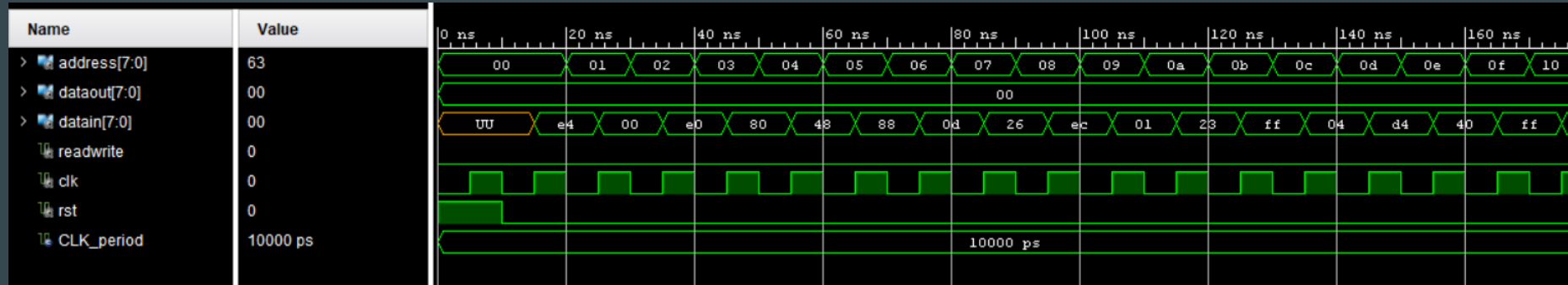

TESTBENCH
RESULTS


REGISTERS

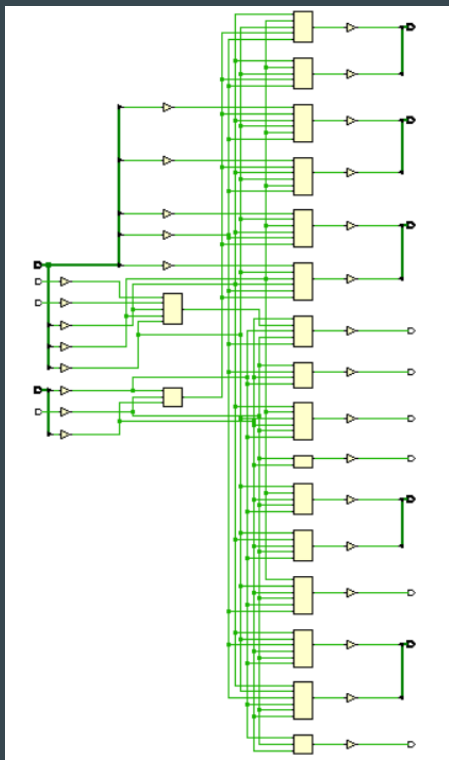- 8-bit, edge-triggered
- Each register in **register_file** entity are within a **registerfs** wrapper
 - **register_file**: It has **dwrite** (acts as enable), **dval** (output of register mux) as input. **zero**, **negative** and registers **r0** – **r3** are the output.
 - **Registerfs**: Synchronous and registers are updated on rising edge of clock.



SYNTHESIZED
DESIGN

REGISTERS (cont'd)

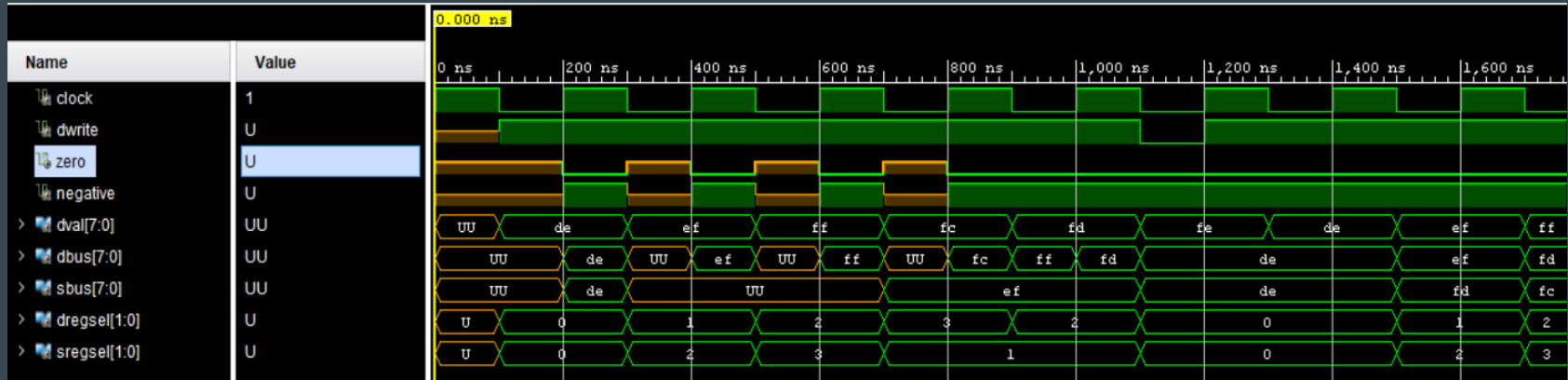

TESTBENCH
RESULTS

ALU

- Two 8-bit inputs **A** and **B** and one 2-bit **aluop** selector
- One 8-bit **result** vector

```
when "10" =>
  res := to_integer(signed(A)) + to_integer(signed(B));
  result <= std_logic_vector(to_signed(res,8));

when "11" =>
  temp1 := resize(signed(A),temp1'length);
  temp2 := resize(signed(B),temp2'length);
  tempr := temp1 - temp2;
  result <= std_logic_vector(resize(signed(tempr),result'length));

when others =>
  result <= A;

end case;
end process;
end Behavioral;
```

ALU (cont'd)

| | | 0.000 ns | | | | | | | | | | | | | | | | | | | | | | | |
|---------------|-------|----------|----|----|----|--------|----|----|----|----------|----|----|----|----------|----|----|----|----------|----|----|----|----------|----|----|----|
| Name | Value | 0 ns | | | | 500 ns | | | | 1,000 ns | | | | 1,500 ns | | | | 2,000 ns | | | | 2,500 ns | | | |
| > A[7:0] | UU | 0f | 03 | 0f | 03 | 83 | 03 | 83 | 82 | 0f | 03 | 0f | 03 | 83 | 82 | 0f | 03 | 0f | 03 | 83 | 82 | 0f | 03 | 83 | 82 |
| > B[7:0] | UU | 0f | 02 | 0f | | 02 | | 81 | 0f | 02 | 0f | | 02 | | 81 | 0f | 02 | 0f | | 02 | | 81 | 0f | | |
| > result[7:0] | UU | 0f | 02 | 0f | 03 | 85 | 05 | 81 | 01 | 0f | 02 | 0f | 03 | 85 | 05 | 81 | 01 | 0f | 02 | 0f | 03 | 85 | 05 | 81 | 01 |
| > aluop[1:0] | U | 0 | | 1 | | 2 | | 3 | | 0 | | 1 | | 2 | | 3 | | 0 | | 1 | | 2 | | 3 | |


TESTBENCH
RESULTS

DECODE LOGIC

- Controlling logic of the simulation
- Contains four multiplexor components and one `jump_logic` component
- Breaks instructions down into their individual components
- Maps the components to the muxes, selects output and returns it


```
34 entity decode_logic is
35   Port (
36       instruction : in  STD_LOGIC_VECTOR (7 downto 0);
37       zero        : in  STD_LOGIC;
38       negative    : in  STD_LOGIC;
39       rst1        : in  STD_LOGIC;
40       stage       : in  STD_LOGIC_VECTOR (1 downto 0);
41       addrsel     : out STD_LOGIC_VECTOR (1 downto 0);
42       irload      : out STD_LOGIC;
43       imload      : out STD_LOGIC;
44       regsel      : out STD_LOGIC_VECTOR (1 downto 0);
45       dwrite      : out STD_LOGIC;
46       aluop       : out STD_LOGIC_VECTOR (1 downto 0);
47       readwrite   : out STD_LOGIC;
48       pcsel       : out STD_LOGIC;
49       pload       : out STD_LOGIC;
50       sregsel     : out STD_LOGIC_VECTOR (1 downto 0);
51       dregsel     : out STD_LOGIC_VECTOR (1 downto 0);
52   );
53 end decode_logic;
```

DECODE LOGIC (cont'd)

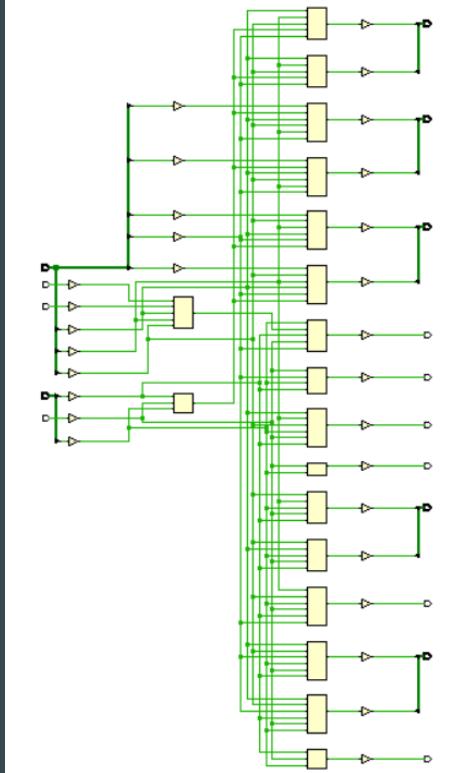


SYNTHESIZED
DESIGN

ELABORATED
DESIGN

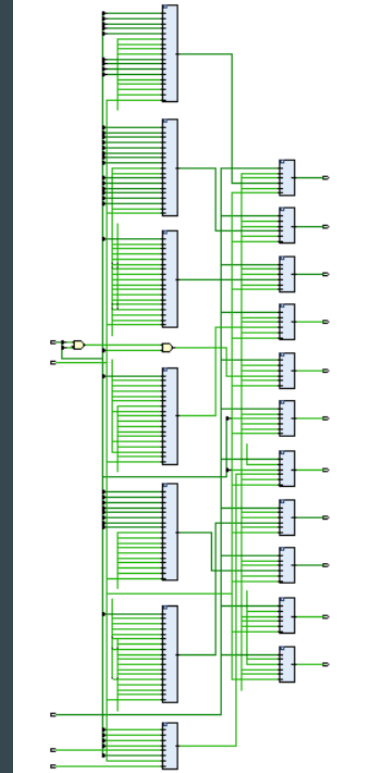

DECODE LOGIC (cont'd)

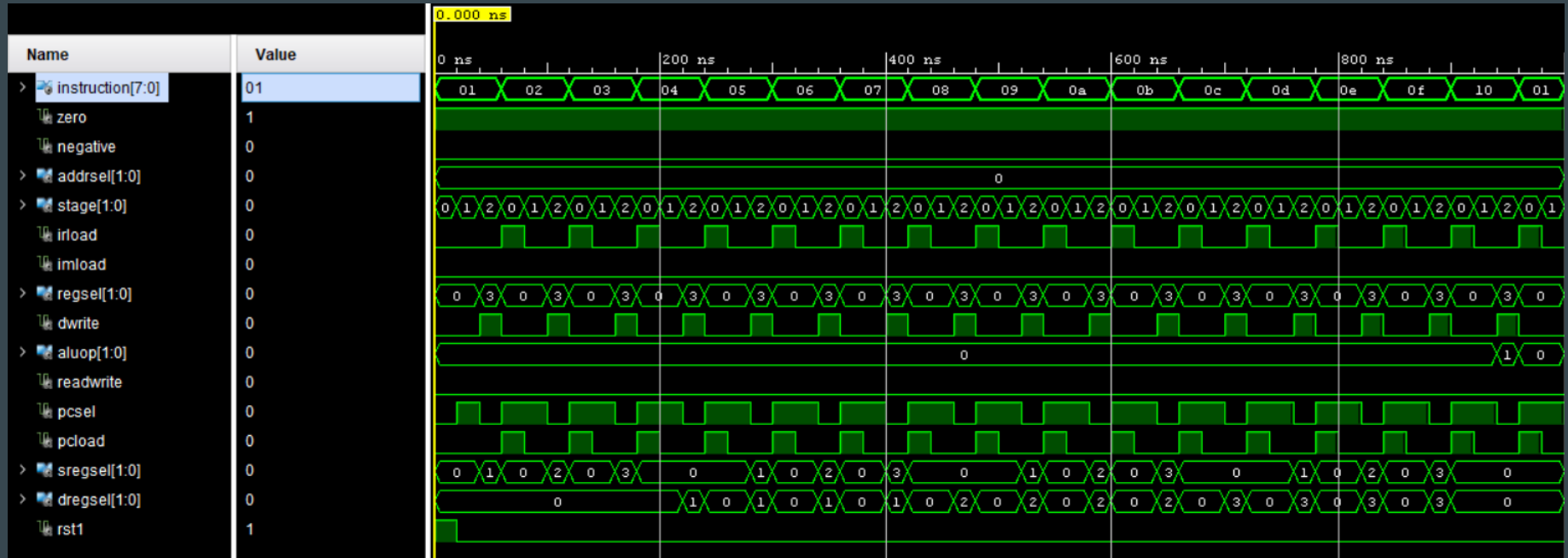


TESTBENCH


RESULTS

MICROCONTROLLER

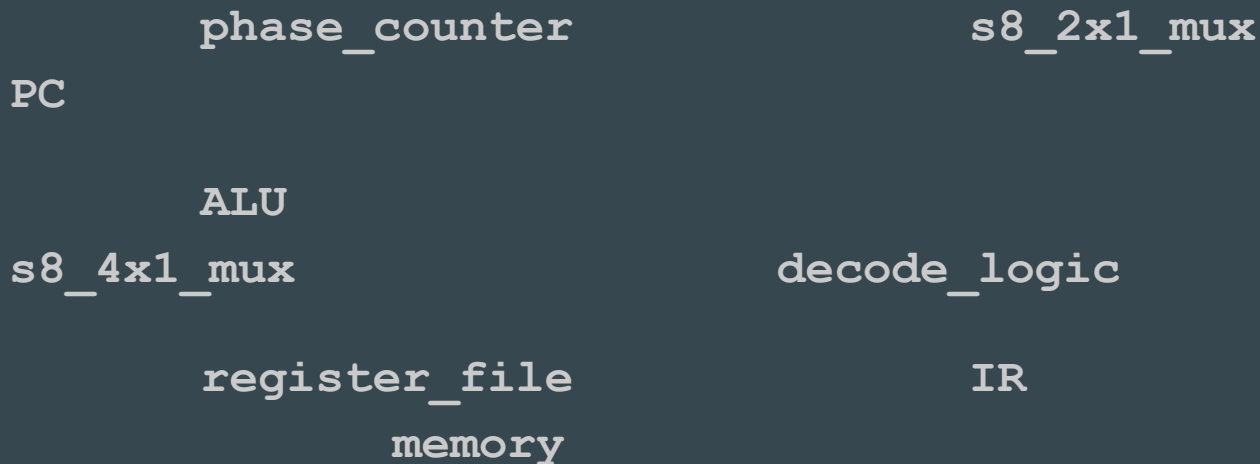
- Highest level of simulation, connects all lower-level outputs to muxes
- Components within the architecture:



MICROCONTROLLER (cont'd)

 

SYNTHESIZED
DESIGN

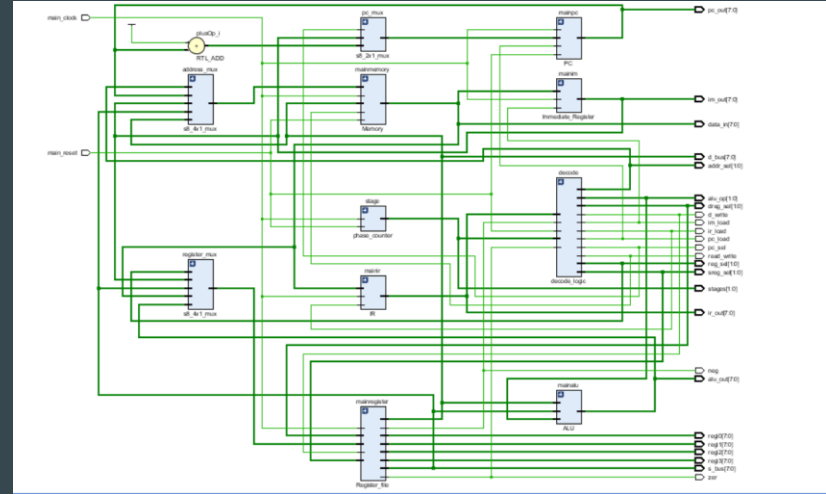

ELABORATED
DESIGN

ISSUES FACED

- Stage counter was unlike normal counter (increments after reset 0 value). In Stage counter, the counter should start from 0 after reset.(During reset counter is 0. So the counter value should be in the following manner if we reset the counter first:


| | Reset | Stages |
|----------------|-------|------------------|
| Normal counter | 0 | 1 2 3 |
| Stage Counter | 0 | 0 1 2 0 1 2 |

- Understanding output of IR and IM register. The output of IR and IM registers were delayed by one clock cycle. That is, the output of stage 0 was found during next clock cycle (stage 1) in IR and the output of stage 1 was found during stage 2 in IM register.

EXAMPLE CODE

| | |
|-------------|-------|
| LI R1,0x00 | e4 00 |
| LI R0,0x80 | e0 80 |
| LW R2, (R0) | 48 |
| JEQ R2, end | 88 0d |
| ADD R1, R2 | 26 |
| LI R3, 0x01 | ec 01 |
| ADD R0, R3 | 23 |
| JMP loop | ff 04 |
| SW R1, 0x40 | d4 40 |
| JMP inf | ff 0f |


MICROCONTROLLER (cont'd)

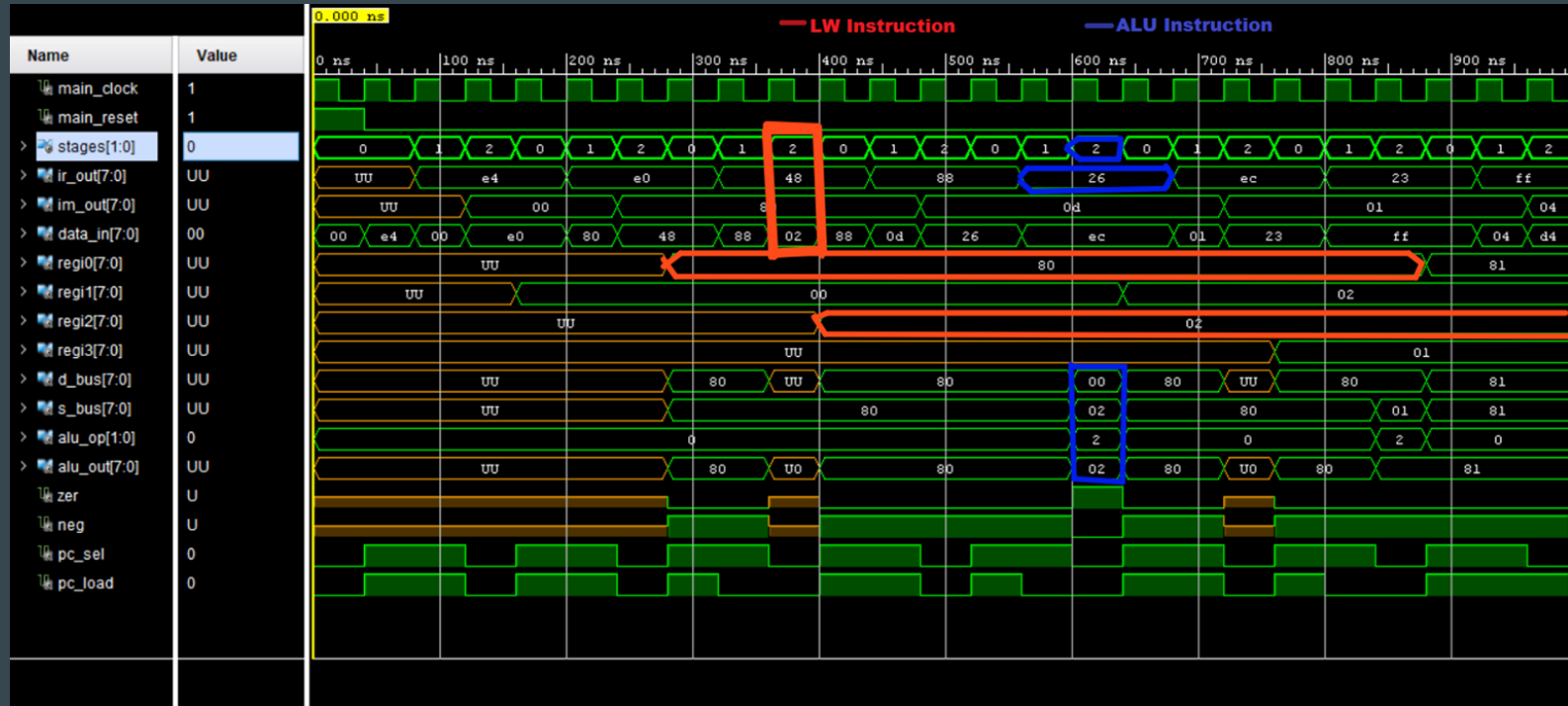

WAVEFORM

RESULTS


MICROCONTROLLER (cont'd)

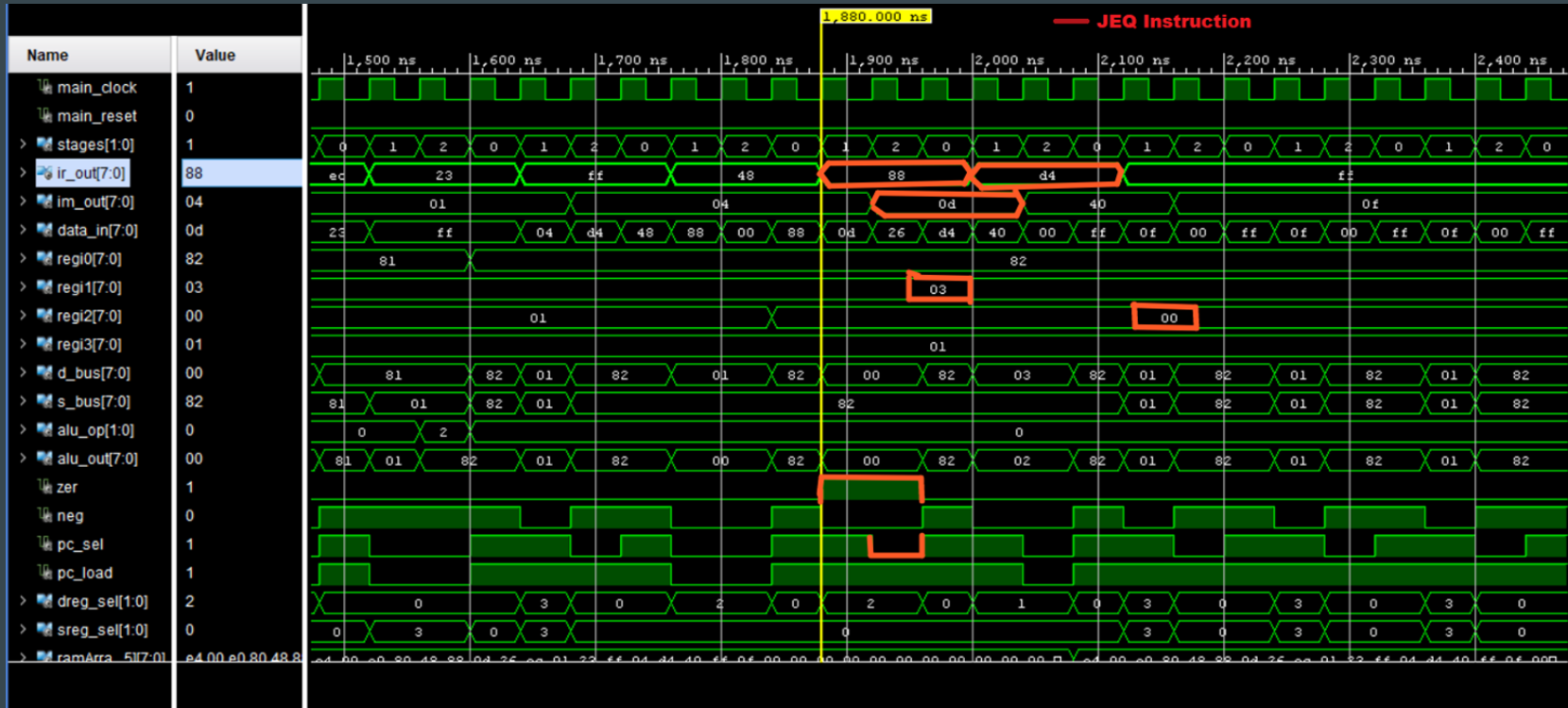

WAVEFORM

RESULTS

MICROCONTROLLER (cont'd)

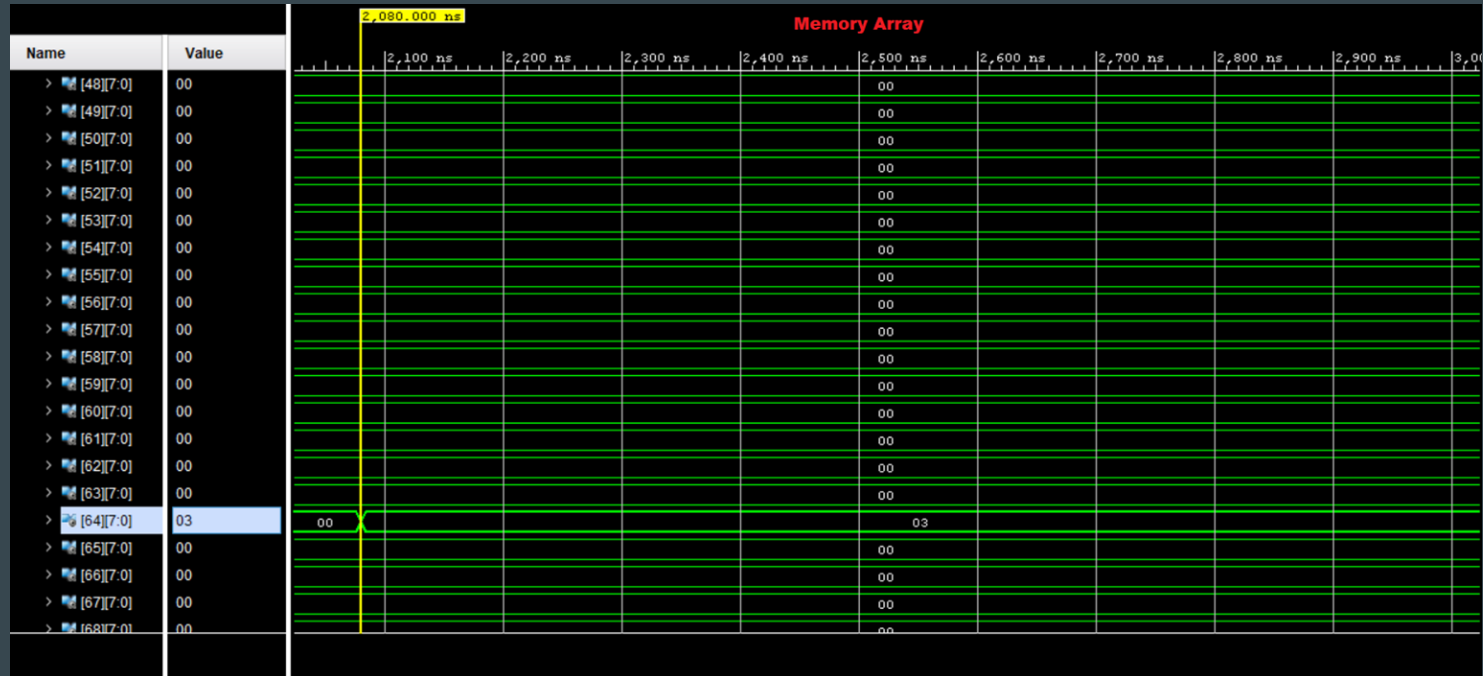

WAVEFORM

RESULTS

QUESTIONS?